

C → storage of flow & (current i , velocity v)

$$q(t) = \int_0^t i(\tau) d\tau + i(0) \quad \dot{q}(t) = i(t)$$

$$e = e(q)$$

examples

Capacitor:	$\dot{q} = i$	$u = \frac{1}{C} q$
spring	$\dot{x} = v$	$F = \frac{1}{1/x} x$



↑
preferred causality

state: generalized position q (q, \dot{q})

\dot{q} for linear element:
effort (u, F)

I

→

storage of effort e

(voltage u , force F)

②

$$x(t) = e(t_0) + \int_{t_0}^t e(z) dz \quad \underline{u} \quad \dot{x}(t) = e(t)$$

$$x = f(x)$$

examples: inductor


$$\dot{\phi} = u$$

$$\dot{i} = \frac{1}{L} \phi$$

mass

$$\dot{x} = F$$

$$v = \frac{1}{m} F$$

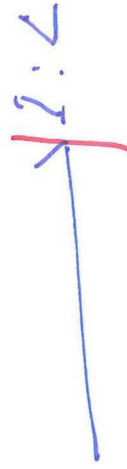

preferred connectivity

state: generalised momentum p
(ϕ, v)

\underline{u} for linear element: $\frac{1}{L}$
flow (i, v)

3

$k \rightarrow$ Fermi level energy

$$e = n(f)$$

examples

resistor

diode

$$u = R_i$$

$$F = 30$$

$\rightarrow R: R$

④


1-junction

→ same flow
(i, v)

n series

same f

$$\Sigma P_{in} = \Sigma P_{out}$$

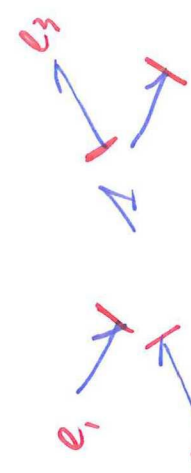

$$Q_4 = P_1 + P_2 - P_3$$

all around ~~nodes~~ ^{nodes} at 1 junction
 $\Sigma \text{ except } 1$


0-junction

→ same effort
(u, F)


n parallel

same e

$$\Sigma f_{in} = \Sigma f_{out}$$

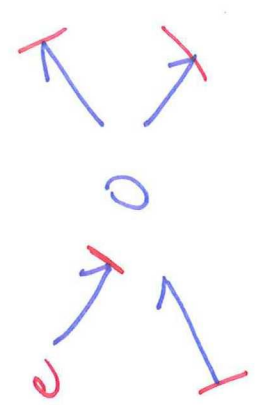

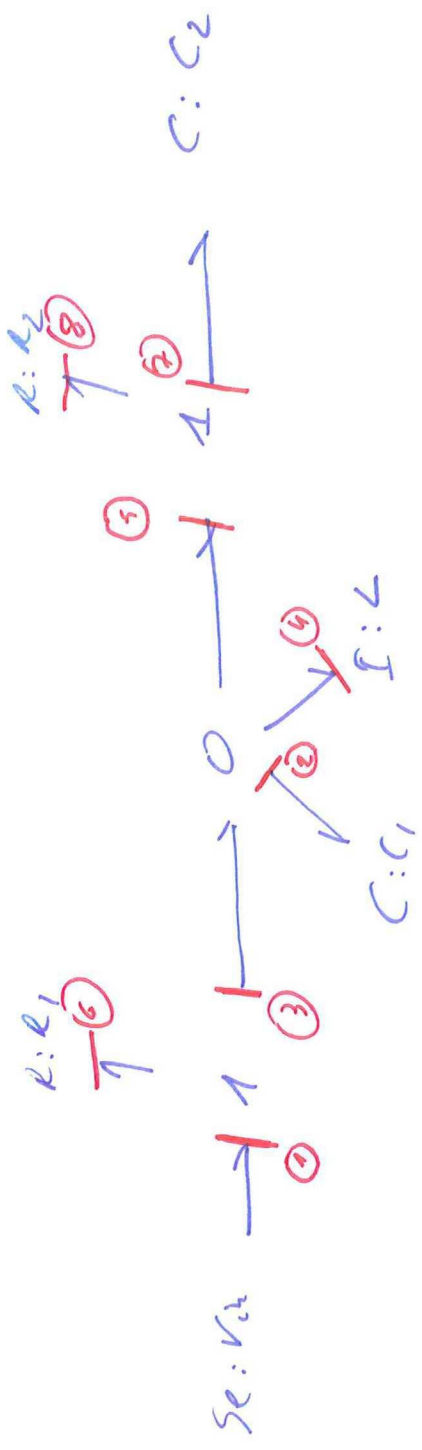exactly 1 around ~~node~~ ^{node} at 0 junction



① : S_e
 ② : preferred causality for C-element

③, ④, ⑤ : 0-junction

⑥ : 1-junction

⑦ : preferred causality for C-element

⑧ : 1-junction

→ Causal, well defined
 → all C/I elements have preferred causality
 → 3 states


⑥

$$\dot{u}_C = \frac{1}{C} i_C$$

$$\dot{i}_L = \frac{1}{L} u_L$$


$R: R_2$
 $u_{C1} - u_{C2}$

\Rightarrow efforts u

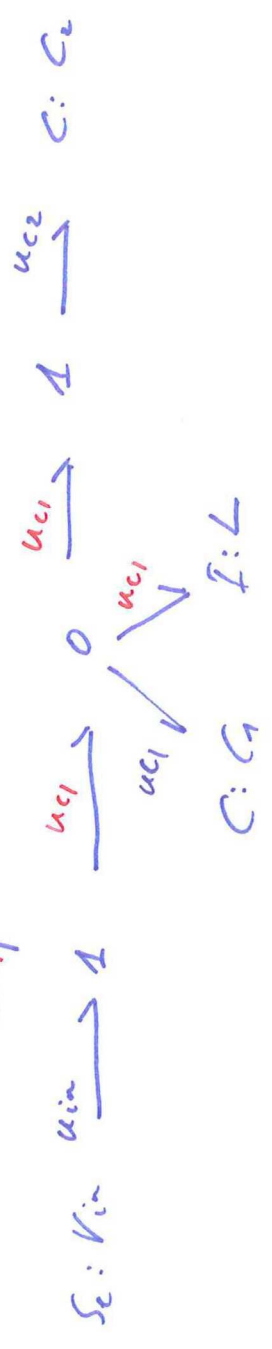

$R: R_L$
 i_{C1}^*

\Rightarrow flows i

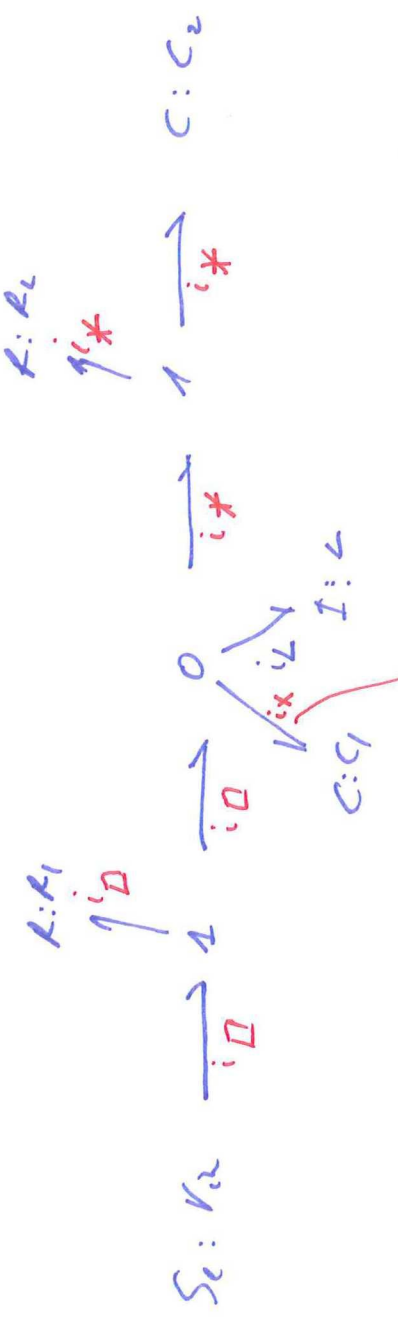

$$i_Q = i_x + i_L + i_{C1}^* \Rightarrow i_x = i_Q - i_L - i_{C1}^*$$

$u = R i$

$$R_1: i_{R1} = \frac{u_{in} - u_{C1}}{R_1} = i_Q$$

$$R_2: i_{R2} = \frac{u_{C1} - u_{C2}}{R_2} = i_{C1}^*$$

7

$$C_1: \dot{u}_{c1} = \frac{1}{C_1} \left(\frac{u_{in} - u_{c1}}{R_1} - \frac{u_{c1} - u_{c2}}{R_2} - i_L \right)$$


$$C_2: \dot{u}_{c2} = \frac{1}{C_2} \frac{u_{c2} - u_{c1}}{R_2}$$

$$L: \dot{i}_L = \frac{1}{L} u_{c1}$$

$$\begin{bmatrix} \dot{u}_{c1} \\ \dot{u}_{c2} \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} \frac{1}{C_1} \left(-\frac{1}{R_2} - \frac{1}{R_1} \right) & \frac{1}{R_2 C_1} & 0 \\ -\frac{1}{R_2 C_2} & \frac{1}{R_2 C_2} & 0 \\ -\frac{1}{L} & 0 & 0 \end{bmatrix} \begin{bmatrix} u_{c1} \\ u_{c2} \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{C_1 R_1} \\ 0 \\ 0 \end{bmatrix} u_{in}$$

$$\dot{x} = Ax + Bu$$

state space model
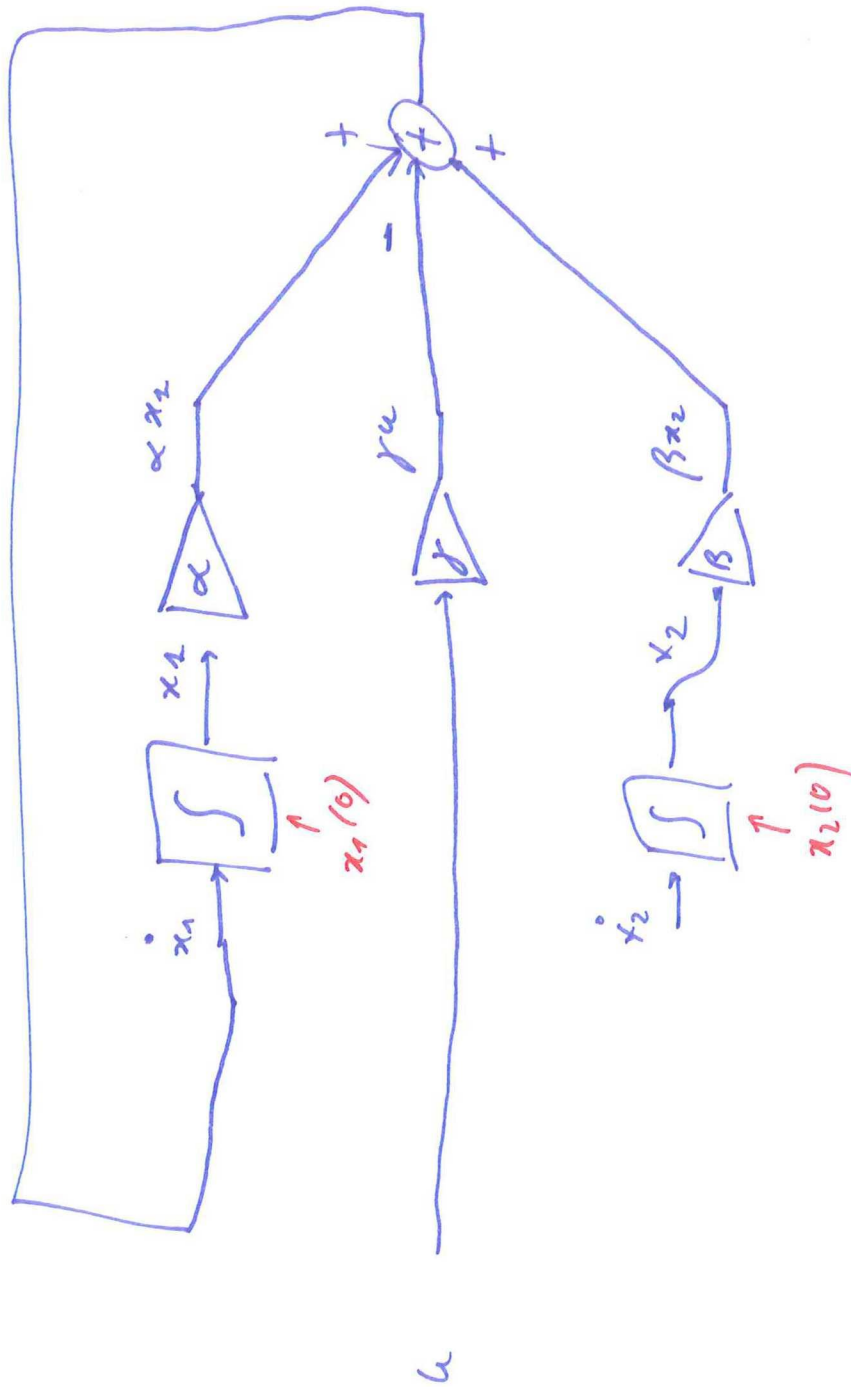
$$x_1 = \alpha x_1 + \beta x_2 - \gamma u$$


9

$$\frac{I_1}{I_2} > I: I_{eq} = \frac{I}{n^2 + 2}$$

$$I_{eq} = ?$$

$$\frac{I_1}{I_{eq}} = I_1$$

$$\frac{I_1}{I_2} > I: I$$

$$\frac{n}{T \cdot F}$$

$$\frac{I_2}{I_1}$$

$$\frac{I_2}{I_1} > 0 \quad e_1 \sqrt{I_3} \quad I: I$$

$$\frac{I_1}{I} = I_3 \quad (a)$$

$$I_1 = I_2 + I_3$$

$$\frac{I_2}{I} = I_4 \quad (5)$$

$$I_2 = n \cdot I_4 \quad (2)$$

$$I_2 = n \cdot e_1 \quad (2)$$


$$\begin{aligned} I_2 &= n \cdot I_4 \quad (5) \\ &= \frac{n \cdot I_2}{I} \quad (5) \\ &= \frac{n^2 \cdot I_1}{I} \quad (2) \end{aligned} \quad (b)$$

$$I_{eq} = \frac{I}{n^2 + 2}$$

$$= \frac{n^2 \cdot e_1 + I_1}{I}$$


$$= \frac{n^2 + 1 \cdot e_2}{I}$$

$$I_1 = I_2 + I_3 \quad (5) \quad (6)$$

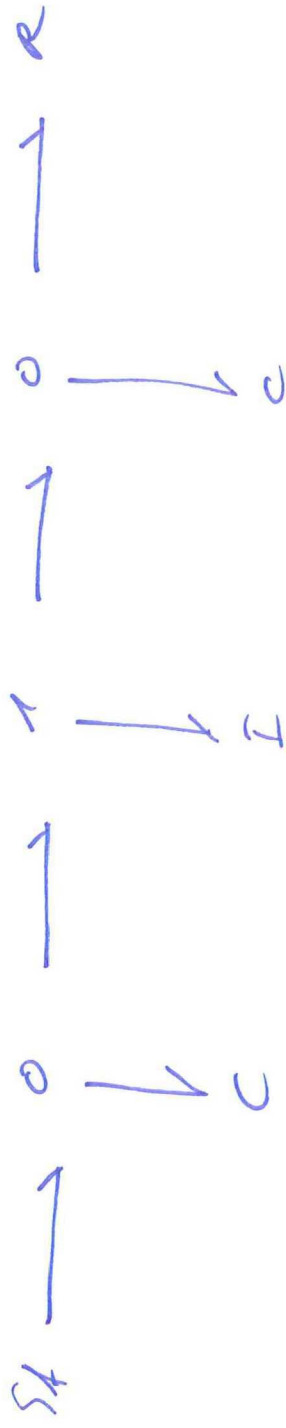

Causality!

states?

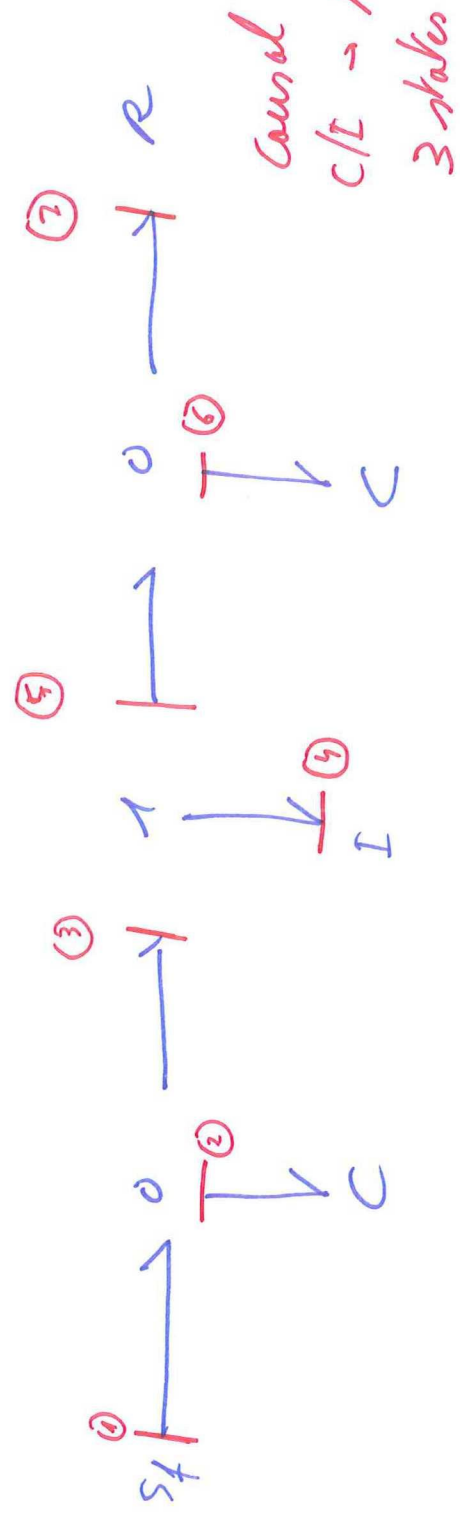

Causal
C/I → preferred causality
3 states

What if Se instead of S4?

→ 1 C element will not get its preferred causality